
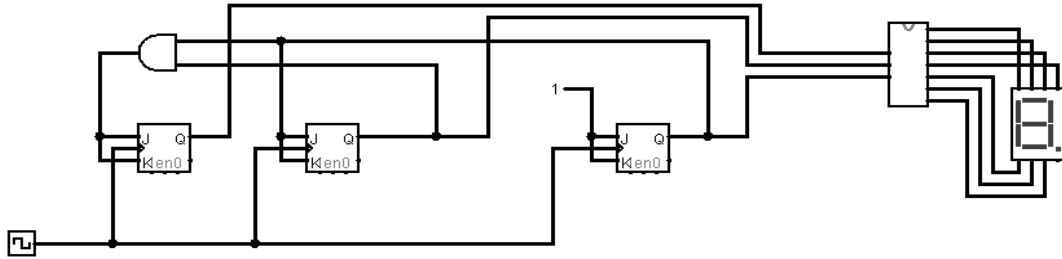



Compteur modulo 8 : 0,1,...,7

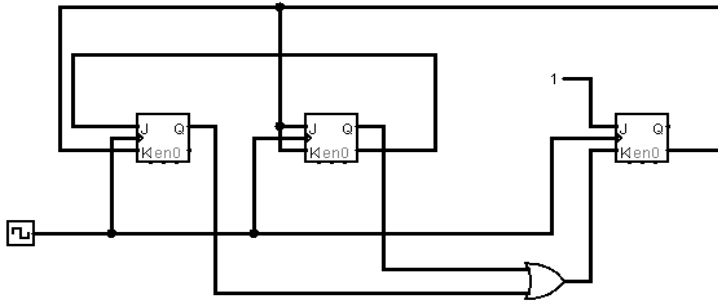


Compteur 5, 4, 3, 2, 1, 5




Compteur modulo 8 : 0,1,...,7

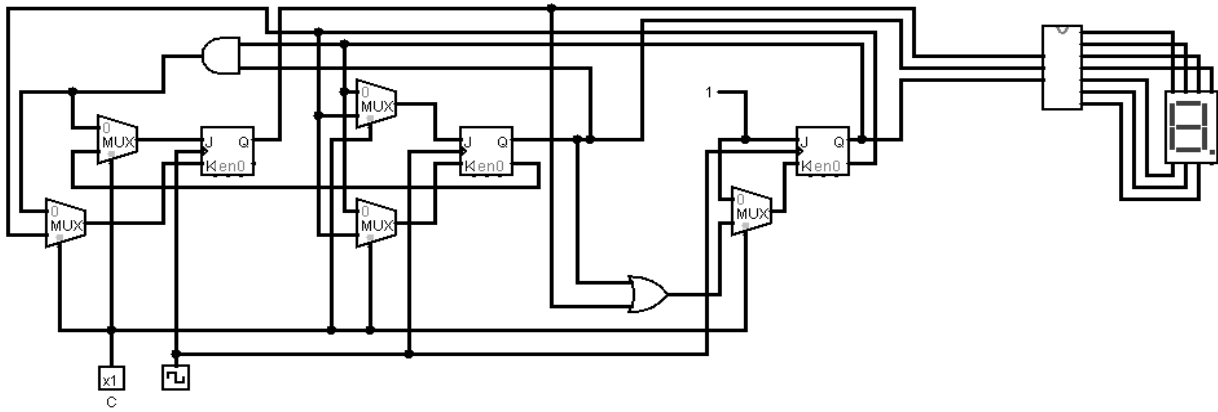

Compteur 5, 4, 3, 2, 1, 5

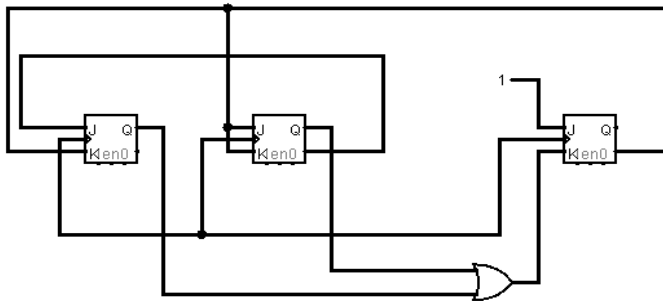

Compteur 0,2,7,6,4,2

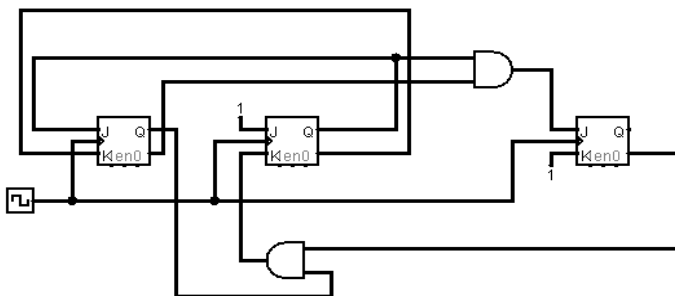

Circuit du décodeur

